

B.C.A Part-I (Semester-I) (CBCS) Examination
1BCA4

FUNDAMENTALS OF ELECTRONICS IN COMPUTER SCIENCE

Time : Three Hours]

[Maximum Marks : 80

Note :— (1) Question no. 1 is compulsory.

(2) Draw neat diagram wherever necessary.

1. (A) Choose the correct alternative & rewrite the sentence :

(i) Which of the following is not a binary Number?

- | | |
|-----------|---------|
| (a) 10101 | (b) 000 |
| (c) 1A1 | (d) 111 |

(ii) The Octal equivalent of 1100101. 001010 is ____.

- | | |
|------------|------------|
| (a) 145.12 | (b) 145.21 |
| (c) 154.12 | (d) None |

(iii) The output of a NOR gate is High if the input is ____.

- | | |
|----------------------|-------------|
| (a) All High | (b) All Low |
| (c) Both (a) and (b) | (d) None |

(iv) How many combinations are there for 3 input gates ?

- | | |
|-------|-------|
| (a) 2 | (b) 4 |
| (c) 6 | (d) 8 |

(v) The Boolean function $A+AB$ is a reduce form of ____.

- | | |
|--------------|------------------|
| (a) $AB+BC$ | (b) $(A+C)(A+B)$ |
| (c) $B(A+C)$ | (d) None |

(vi) Select line required for 16 : 1 MUX is ____.

- | | |
|-------|-------|
| (a) 3 | (b) 4 |
| (c) 5 | (d) 8 |

(vii) Race around condition occurs in ____ FF.

- | | |
|--------|----------|
| (a) JK | (b) JKMS |
| (c) D | (d) T |

(viii) In SRFF, if $Q=0$, the output is said to be ____.

- (a) Set (b) Reset
- (c) Invalid (d) None

(ix) Asynchronous counter is also called as ____ counter.

- (a) Serial (b) Parallel
- (c) Ripple (d) None

(x) In ____ counter the clock is applied to all Flip-Flop simultaneously.

- (a) Synchronous (b) Asynchronous
- (c) Serial (d) None

10×1=10

(B) Fill in the blanks :

- (i) 2'S complement of binary number 101011 is ____.
- (ii) A full adder circuit has ____ inputs.
- (iii) Multiplexer is also called as ____.
- (iv) To avoid Race around condition ____ FF is used.
- (v) To make a 8 bit counter we require ____ FF.

5

(C) Answer in one sentence :

- (i) What is the base of binary & hex number system ?
- (ii) Which gates are called as basic logic gates?
- (iii) Write Boolean expression of De-Morgan's First & second theorem.
- (iv) What is meant by Toggle output?
- (v) What is synchronous counter?

5

2. (A) Explain decimal to binary & binary to decimal conversion with example.

8

(B) Perform the following binary arithmetic operations :

4

(1) $101011 + 10101$

(2) 110110×101

OR

3. (A) Explain decimal, binary & hex number system.

8

(B) Subtract $(11001)_2$ from $(10110)_2$ using 2'S complement method.

4

4. (A) Explain half adder with block & logic diagram.

4

(B) Explain Ex-OR & Ex-NOR logic gates.

8

OR

5. (A) Explain with truth table basic logic gates. 4
 (B) Explain with logic diagram full subtractor. 8
6. (A) Prove that : 4
 (1) $(A+B)(A+C) = A+BC$
 (2) $AB+A(B+C)+B(B+C) = AC+B$
 (B) Explain with logic diagram 1 : 8 De-MUX 8
- OR**
7. (A) State & prove De-Morgan's theorems. 4
 (B) Minimize the function using K-map $Y = \sum m(1, 3, 4, 9, 11, 12)$ 8
8. (A) Explain the working of JK-FF with logic diagram & truth table. 8
 (B) Explain the operation of D-FF using logic diagram, truth table & symbol. 4
- OR**
9. (A) What is race around condition? Explain how JKMS remove this condition. 8
 (B) Explain RS latch using NOR gates. 4
10. (A) Explain 4 bit synchronous up counter with waveform. 8
 (B) Explain operation of shift left register with timing diagram. 4
- OR**
11. (A) Draw block diagram of PISO shift register and explain its working. 8
 (B) Explain 4 bit asynchronous down counter. 4